

**Problem 5**  
**SZABÓ Attila 11th Grade**  
**Leőwey Klára High School**  
**Pécs, Hungary**

Let the vertices of the connection be numbered as shown in the figure. Let the potential of the  $k$ th vertex be  $u_k$ , the current flowing from the  $k$ th vertex towards the 0th vertex  $i_k$ , while the current flowing from the  $k$ th vertex to the  $(k+1)$ th one (modulo 4, of course)  $i_{k+4}$  (positive is the current when flowing in the branch in the mentioned direction). The following differential equations between the currents and voltages for specific circuit elements are well-known:

$$\begin{aligned}
 (1) \quad u_1 - u_2 &= L_1 \frac{di_5}{dt} & (5) \quad i_1 &= C_1 \frac{d(u_1 - u_0)}{dt} \\
 (2) \quad u_2 - u_3 &= L_1 \frac{di_6}{dt} & (6) \quad i_2 &= C_1 \frac{d(u_2 - u_0)}{dt} \\
 (3) \quad u_3 - u_4 &= L_2 \frac{di_7}{dt} & (7) \quad i_3 &= C_2 \frac{d(u_3 - u_0)}{dt} \\
 (4) \quad u_4 - u_1 &= L_2 \frac{di_8}{dt} & (8) \quad i_4 &= C_2 \frac{d(u_4 - u_0)}{dt}.
 \end{aligned}$$

From the first law of Kirchhoff the following equations can be got:

$$\begin{aligned}
 (9) \quad i_1 &= i_8 - i_5 \\
 (10) \quad i_2 &= i_5 - i_6 \\
 (11) \quad i_3 &= i_6 - i_7 \\
 (12) \quad i_4 &= i_7 - i_8.
 \end{aligned}$$

It is easy to see, that this system is linear, so it has definite eigenfrequencies. In order to find them, we assume that all quantities depend on time as  $x = X e^{i\omega t}$ , where  $\omega$  denotes the angular eigenfrequency (they always occur in pairs  $(\omega, -\omega)$ , this can be considered as phase difference). Using this substitution in Eqs 1–12, and simplifying with  $e^{i\omega t}$  gives the following equations:

$$\begin{aligned}
 (1) \quad U_1 - U_2 &= i\omega L_1 I_5 & (5) \quad I_1 &= i\omega C_1 (U_1 - U_0) & (9) \quad I_1 &= I_8 - I_5 \\
 (2) \quad U_2 - U_3 &= i\omega L_1 I_6 & (6) \quad I_2 &= i\omega C_1 (U_2 - U_0) & (10) \quad I_2 &= I_5 - I_6 \\
 (3) \quad U_3 - U_4 &= i\omega L_2 I_7 & (7) \quad I_3 &= i\omega C_2 (U_3 - U_0) & (11) \quad I_3 &= I_6 - I_7 \\
 (4) \quad U_4 - U_1 &= i\omega L_2 I_8 & (8) \quad I_4 &= i\omega C_2 (U_4 - U_0) & (12) \quad I_4 &= I_7 - I_8.
 \end{aligned}$$

From Eqs 5–8 the values of  $U_i - U_0$ , consequently  $U_i - U_{i+1}$  can be determined in terms of  $I_i$ , which can be equated with the values from Eqs 1–4. For example,

$$\begin{aligned}
 U_1 - U_2 &= (U_1 - U_0) - (U_2 - U_0) = \frac{I_1}{i\omega C_1} - \frac{I_2}{i\omega C_1} = i\omega L_1 I_5 \\
 \frac{I_8 - I_5}{i\omega C_1} - \frac{I_5 - I_6}{i\omega C_1} &= i\omega L_1 I_5 \\
 (13) \quad -\frac{2}{C_1 L_1} I_5 + \frac{1}{C_1 L_1} I_6 + \frac{1}{C_1 L_1} I_8 &= -\omega^2 I_5.
 \end{aligned}$$

The same calculation for other  $I_k$ s gives

$$(14) \quad -\left(\frac{1}{C_1 L_1} + \frac{1}{C_2 L_1}\right) I_6 + \frac{1}{C_1 L_1} I_5 + \frac{1}{C_2 L_1} I_7 = -\omega^2 I_6$$

$$(15) \quad -\frac{2}{C_2 L_2} I_7 + \frac{1}{C_2 L_2} I_6 + \frac{1}{C_2 L_2} I_8 = -\omega^2 I_7$$

$$(16) \quad -\left(\frac{1}{C_1 L_2} + \frac{1}{C_2 L_2}\right) I_8 + \frac{1}{C_1 L_2} I_5 + \frac{1}{C_2 L_2} I_7 = -\omega^2 I_8.$$

The eqs 13–16 can be written together in the matrix form

$$\begin{pmatrix} -\frac{2}{C_1 L_1} & \frac{1}{C_1 L_1} & 0 & \frac{1}{C_1 L_1} \\ \frac{1}{C_1 L_1} & -\left(\frac{1}{C_1 L_1} + \frac{1}{C_2 L_1}\right) & \frac{1}{C_2 L_1} & 0 \\ 0 & \frac{1}{C_2 L_2} & -\frac{2}{C_2 L_2} & \frac{1}{C_2 L_2} \\ \frac{1}{C_1 L_2} & 0 & \frac{1}{C_2 L_2} & -\left(\frac{1}{C_1 L_2} + \frac{1}{C_2 L_2}\right) \end{pmatrix} \begin{pmatrix} I_5 \\ I_6 \\ I_7 \\ I_8 \end{pmatrix} = -\omega^2 \begin{pmatrix} I_5 \\ I_6 \\ I_7 \\ I_8 \end{pmatrix}.$$

From this form it is easy to see, that the problem is to find the eigenvalues of the matrix on the left hand side: these eigenvalues give the values of  $-\omega^2$ . The characteristic equation of the matrix is (with the help of Maple):

$$\lambda^4 + \left(\frac{1}{L_1 C_1} + \frac{1}{L_2 C_1} + \frac{1}{L_1 C_2} + \frac{1}{L_2 C_2}\right) \lambda^3 + \left(\frac{1}{L_1^2 C_1^2} + \frac{1}{L_2^2 C_2^2} + \frac{2}{L_1 L_2 C_1^2} + \frac{2}{L_1 L_2 C_2^2} + \frac{2}{L_1^2 C_1 C_2} + \frac{2}{L_2^2 C_1 C_2} + \frac{10}{L_1 L_2 C_1 C_2}\right) \lambda^2 + \left(\frac{4}{L_1^2 L_2 C_1^2 C_2} + \frac{4}{L_1^2 L_2 C_1 C_2^2} + \frac{4}{L_1 L_2^2 C_1^2 C_2} + \frac{4}{L_1 L_2^2 C_1 C_2^2}\right) \lambda = 0.$$

From the equation it is obvious that  $\lambda = 0$ , consequently  $\omega = 0$  is a solution: knowing this, we can divide the equation by  $\lambda$ ; in the following, we consider it this way. Now, using the fact that  $L_2 \gg L_1$  and  $C_2 \gg C_1$ , we can ignore the terms containing  $\frac{1}{L_2}$  and  $\frac{1}{C_2}$ . This way, the equation becomes

$$\lambda^3 + \frac{3}{L_1 C_1} \lambda^2 + \frac{1}{L_1^2 C_1^2} \lambda = 0.$$

0 is obviously the solution of the equation, however, this comes from ignoring terms; the other two eigenvalues can be got from the quadratic equation  $\lambda^2 + \frac{3}{L_1 C_1} \lambda + \frac{1}{L_1^2 C_1^2} = 0$ , the roots of which are  $\lambda_1 = -\frac{3+\sqrt{5}}{2} \frac{1}{L_1 C_1}$  and  $\lambda_2 = -\frac{3-\sqrt{5}}{2} \frac{1}{L_1 C_1}$ . Now we have to determine the third root of the equation. From the previous it can be found, that this  $\lambda$  is ignorable compared to  $\frac{1}{L_1 C_1}$ ; this means that higher-order terms can be ignored compared to the two least-order one; the equation then becomes (ignoring the terms ignorable compared to the greatest in each coefficient):

$$\frac{1}{L_1^2 C_1^2} \lambda + \frac{4}{L_1^2 L_2 C_1^2 C_2} = 0$$

$$\lambda_3 = -\frac{4}{L_2 C_2}.$$

Now we have all eigenvalues of the matrix of the system; now we're going to calculate the eigenfrequencies from  $\lambda = -\omega^2$ .

$\lambda_1 = -\frac{3+\sqrt{5}}{2} \frac{1}{L_1 C_1}$ ; from this,  $\omega_1 = \sqrt{\frac{3+\sqrt{5}}{2} \frac{1}{L_1 C_1}} = \frac{1+\sqrt{5}}{2} \frac{1}{\sqrt{L_1 C_1}}$ . From  $\lambda_2 = -\frac{3-\sqrt{5}}{2} \frac{1}{L_1 C_1}$ ,  $\omega_2 = \sqrt{\frac{3-\sqrt{5}}{2} \frac{1}{L_1 C_1}} = \frac{1-\sqrt{5}}{2} \frac{1}{\sqrt{L_1 C_1}}$  comes. Eigenvalue  $\lambda_3 = -\frac{4}{L_2 C_2}$  gives the eigenfrequency  $\omega_3 = \sqrt{\frac{4}{L_2 C_2}} = \frac{2}{\sqrt{L_2 C_2}}$ . We investigate now the case of the fourth eigenfrequency,  $\lambda_4 = 0$ : in this case there is a nonzero eigenvector  $(1, 1, 1, 1)^*$ , meaning that a constant current flows round in the outer ring, and there is no current in the 0th vertex: this is physically able; there is no voltage inducing in the coils, so vertices 1–4 are on the same potential  $u_1$ , while  $u_0$  is independent of this. Thus the angular eigenfrequencies of the circuit are  $\omega_1 = \frac{1+\sqrt{5}}{2} \frac{1}{\sqrt{L_1 C_1}}$ ,  $\omega_2 = \frac{1-\sqrt{5}}{2} \frac{1}{\sqrt{L_1 C_1}}$ ,  $\omega_3 = \frac{2}{\sqrt{L_2 C_2}}$  and  $\omega_4 = 0$ .